



Design of Beetle1.3

Daniel Baumeister, Sven Löchner, Hans Verkooijen





Motivation for Beetle1.3

in descending order of priority:

- ◆ Sticky Charge Effect
- ◆ Comparator Offset Variation
- ◆ 80 MHz Cross Talk
- ◆ Output Driver Performance
- ◆ Sagging Readout Baseline








Sticky Charge Effect (1)

- ◆ signal carry-over from previous event into an empty event, strong baseline drift
- ◆ only present for consecutive readouts, i.e. during a readout operation a further trigger arrives

non-consecutive readout

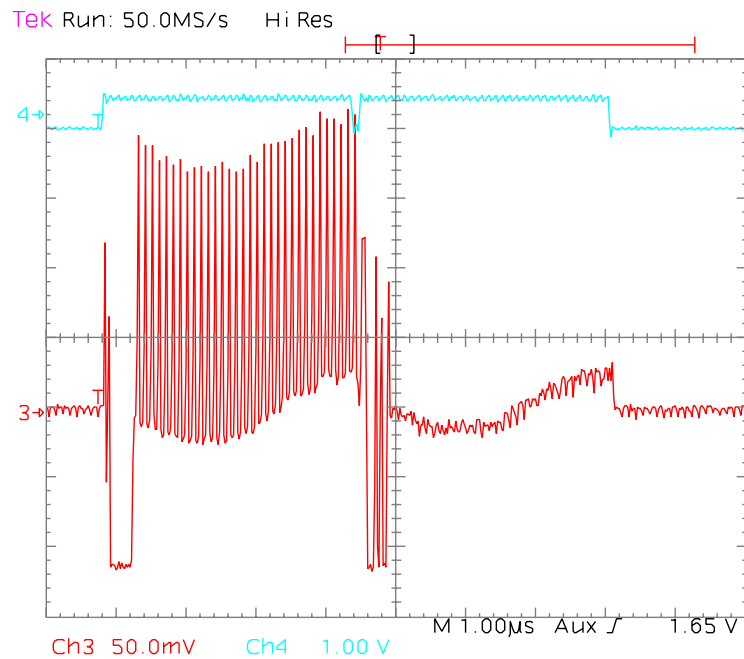


consecutive readout

 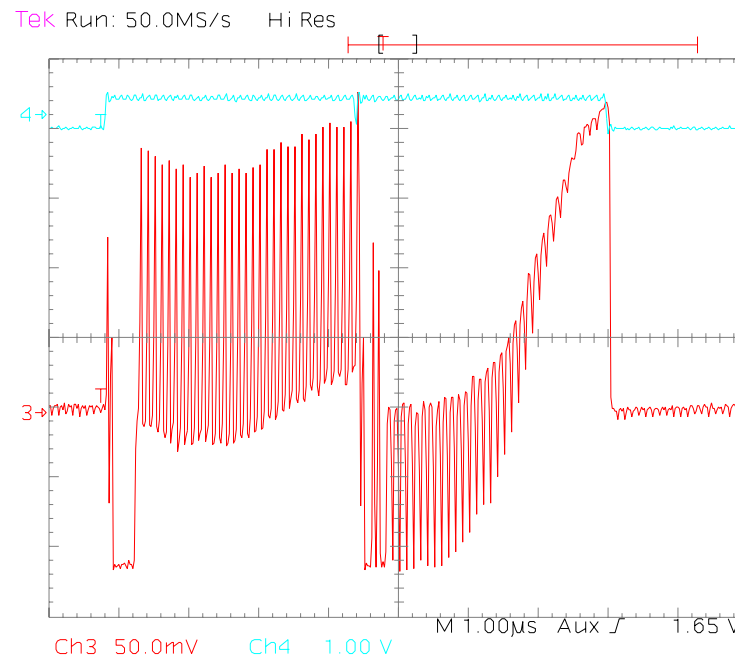


ROampReset

MuxTrack

 



ROampReset

MuxTrack

 



Sticky Charge Effect (3): Simulations

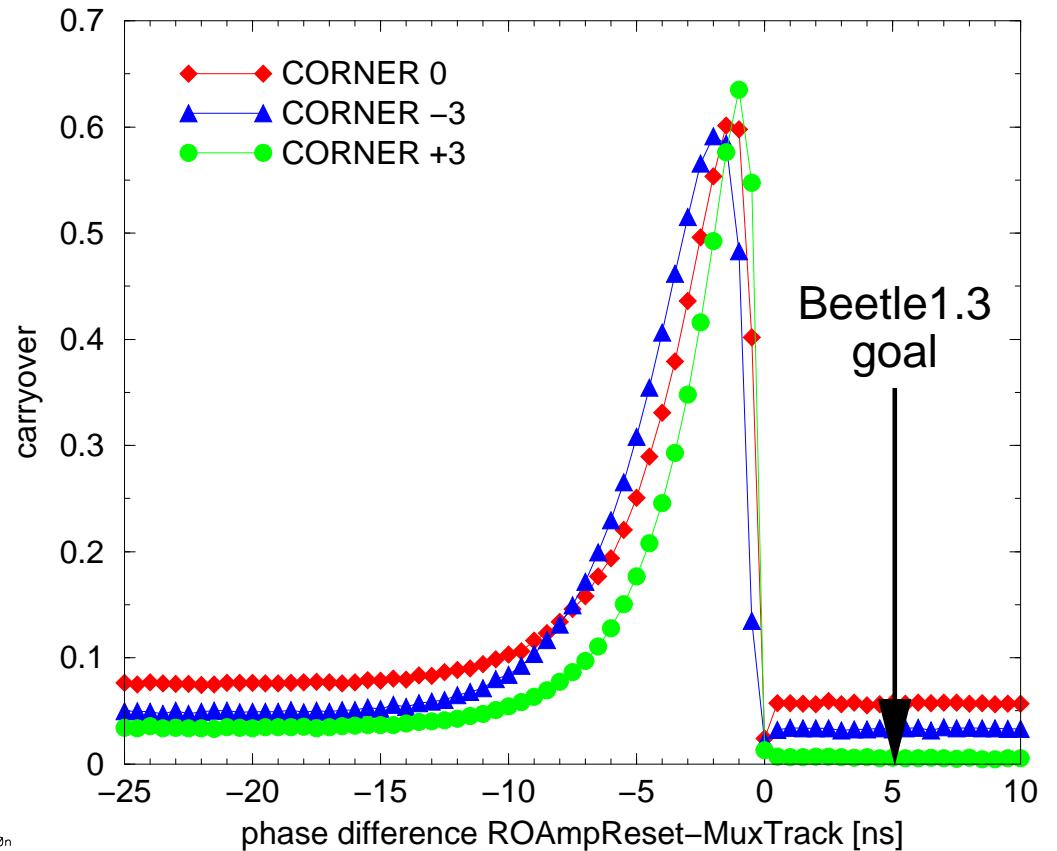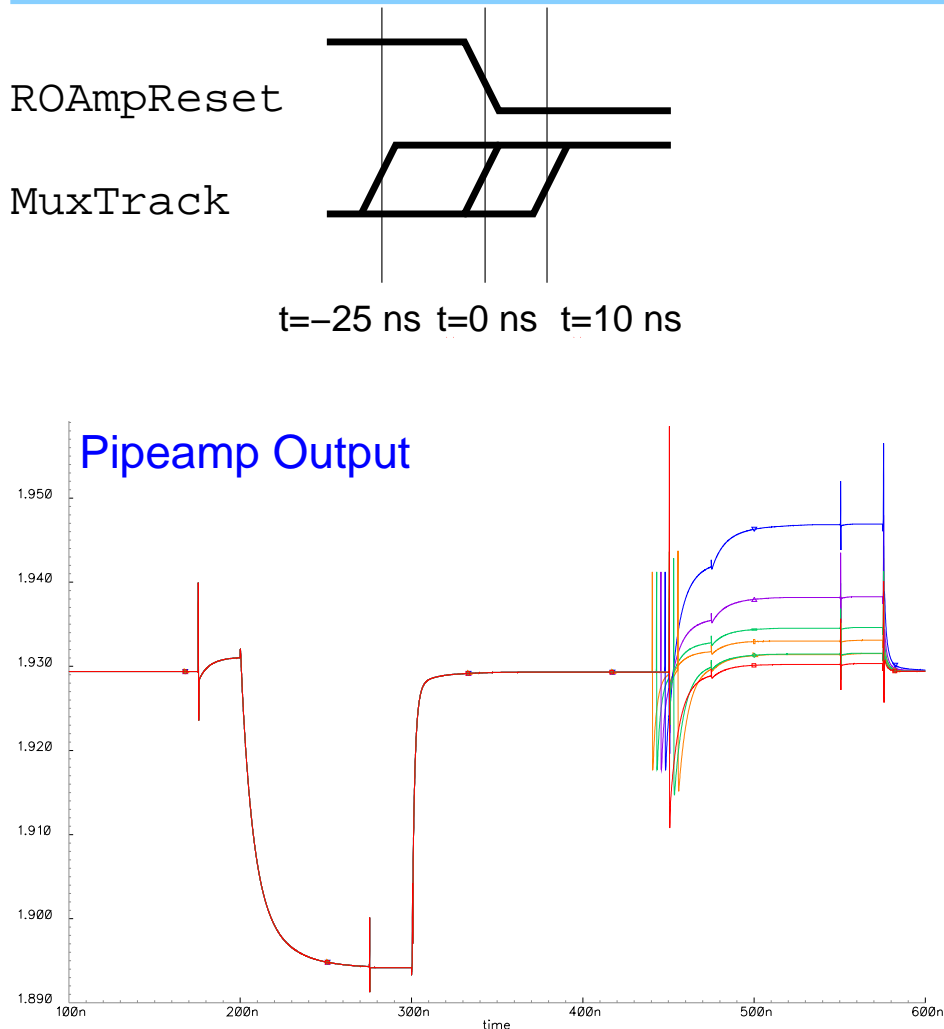


Modification in Beetle1.3: analog delay of MuxTrack by 5 ns ↑





Sticky Charge Effect (4)

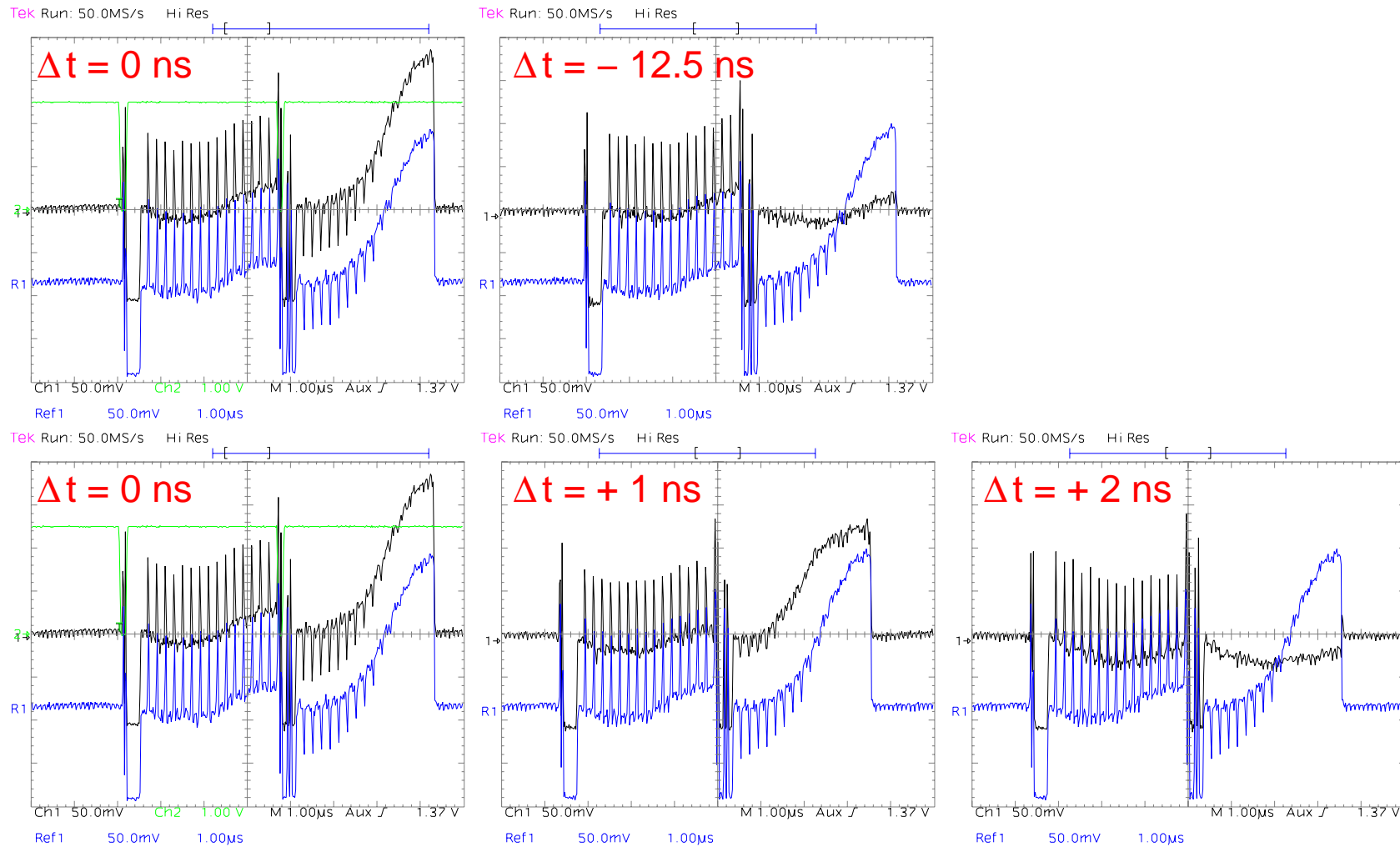probe needle test with pos. and neg. phase shift






Comparator Changes

Motivation: offset–spread: $\sigma = 2.4$ DAC units = 300 nA = 0.2 MIP

- ◆ bipolar
- ◆ too large for compensation with present DACs for channel threshold

Measures:

 - ◆ merging input buffers: reduces additional offset
- ◆ gain increase of buffer: reduces influence on offset
- ◆ increase resolution of threshold current to 5 bits
required: ± 900 nA = ± 0.6 MIP





80 MHz X-talk

cross talk with a frequency spectrum of 80 MHz

present on

digital signals, e.g. DataValid

analogue signals, e.g. AnalogOut

power supply lines: Vdd, Vdda

comparison:

flip-flops:

clock buffers:

guard rings logic core:

Beetle1.1

1349

21


analogue

Beetle1.2

3043

284



digital

 

Possible solutions:


reduced no. of clock buffers

on-chip power blocking

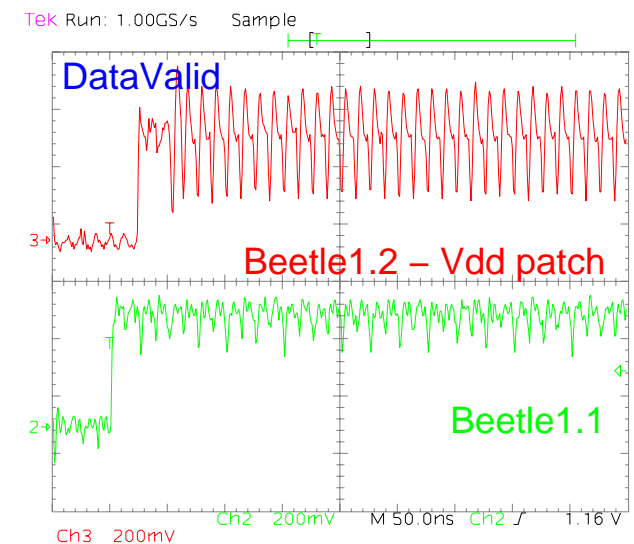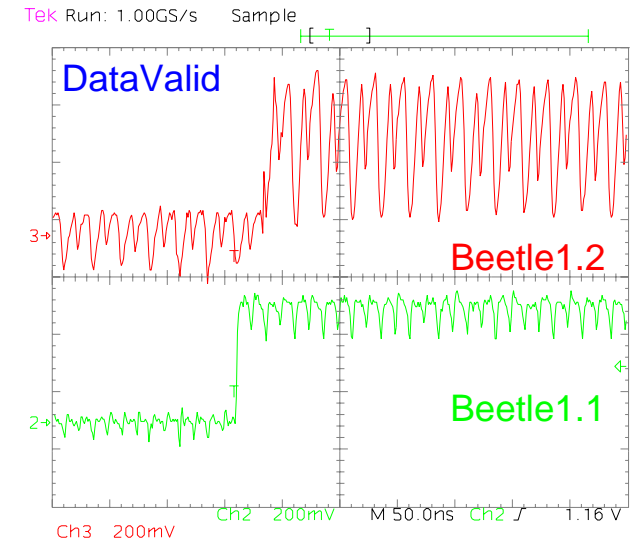





Readout Baseline Variation

 

Observation:
shaper bias current affects
amplitude of baseline variation

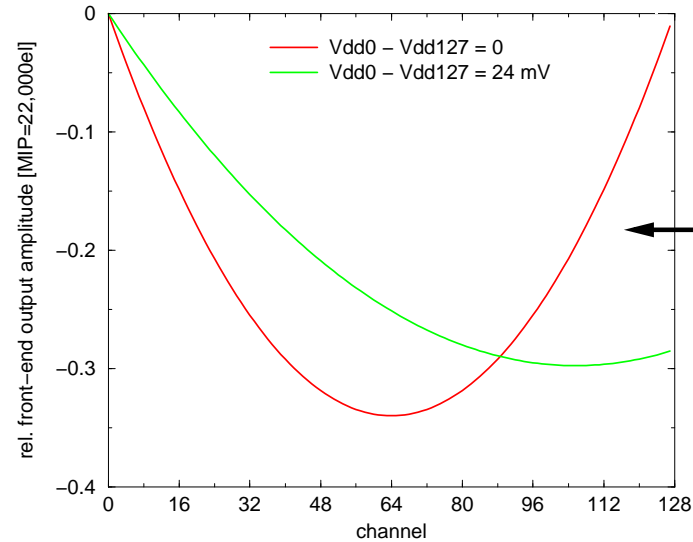 Laser Patch: \longrightarrow
probing shaper power supply
at various channels



difference in VDD between
ch.0 and ch.127: 24 mV

\longleftarrow Simulation:
resistive VDD-network in shaper

**Modification in Beetle1.3: additional power supply lines
in shaper (+ 100 um)**





Modifications in Beetle 1.3

Design Changes (on schematic level)

- ◆ analogue delay of MuxTrack signal fix of sticky charge effect
- ◆ improved comparator 5 bit channel threshold resolution
- ◆ Current Output Buffer increased gain, diff. output current
- ◆ Mux: Switch Control reduction of switching spikes
- ◆ Control Logic bug fixes (daisy chain op., low-Rclk op.)
- ◆ new I2C-Pads 5V compatible
- ◆ modified test pulse pattern "+1/-1" pattern

X-talk Measures

- ◆ reduced no. of FF in multiplexer by factor 3 (414 → 138)
- ◆ reduced no. of clock buffers in logic core 275 → 104
- ◆ on-chip power blocking





Modifications in Beetle 1.3

Layout and Power Routing Issues

- ◆ modified front-end power pads
(power and ground at top and bottom of chip)
- ◆ improved shaper power routing
- ◆ improved front-end biasing scheme
- ◆ separation of comparator core and LVDS pad power
- ◆ improved pipeamp power routing
- ◆ separation of power supply of multiplexer and logic core
- ◆ introduction of bias generator probe pad
- ◆ implementation of 2 new power pads for logic core
(located at bottom side)
- ◆ merged pad openings of adjacent power pads
- ◆ on-chip power blocking in total 1375 gate caps: ~ 0.9 nF
- ◆ improved guard ring structures n-well and substrate contacts


This all together increased chip size by 300 um in x-direction
(now: 5400 x 6100 um²)



Testpulse / Front-end

Testpulse

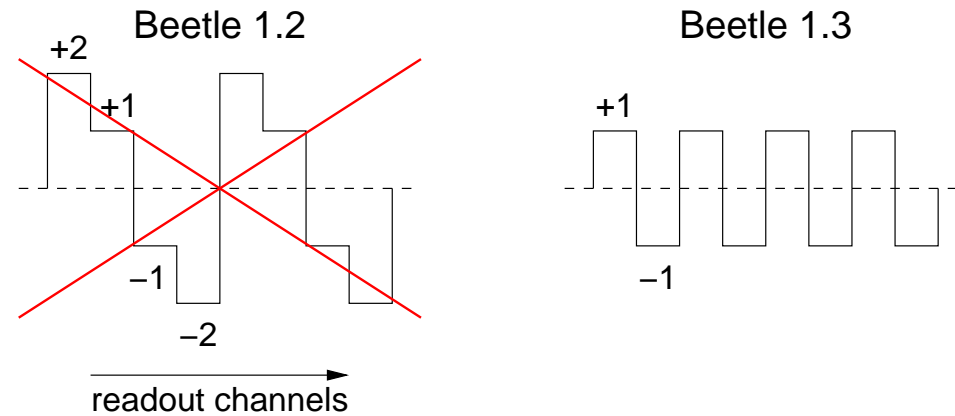- reduced testpulse pattern (+1 / -1)
- improved guardring structure



Front-end



- revised power routing (esp. Shaper)
- decoupling capacitors in Buffer (1.3pF/ch)
- modified bias schema
- improved guardring structure

	resistances	Beetle 1.2 [mOhm/ch.]	Beetle 1.3 [mOhm/ch.]
power:	Rpreamp	13.83	12.37
	Rshaper1	39.21	11.17
	Rshaper2	70.24	
	Rbuffer	137.70	39.69
bias:	Rprebias	478.64	151.78
	Rprebias1	690.40	278.26
	Rshabias	1569.02	492.94
	Rshabias1	650.30	201.31
	Rbufbias	1569.02	985.88

Front-end



Front-end simulation

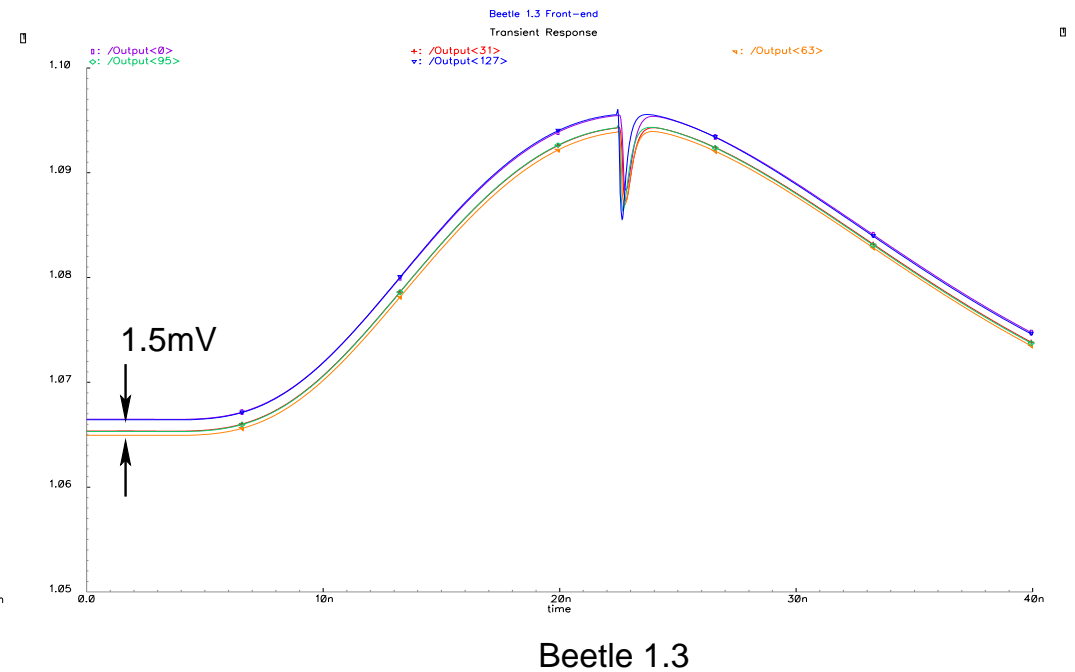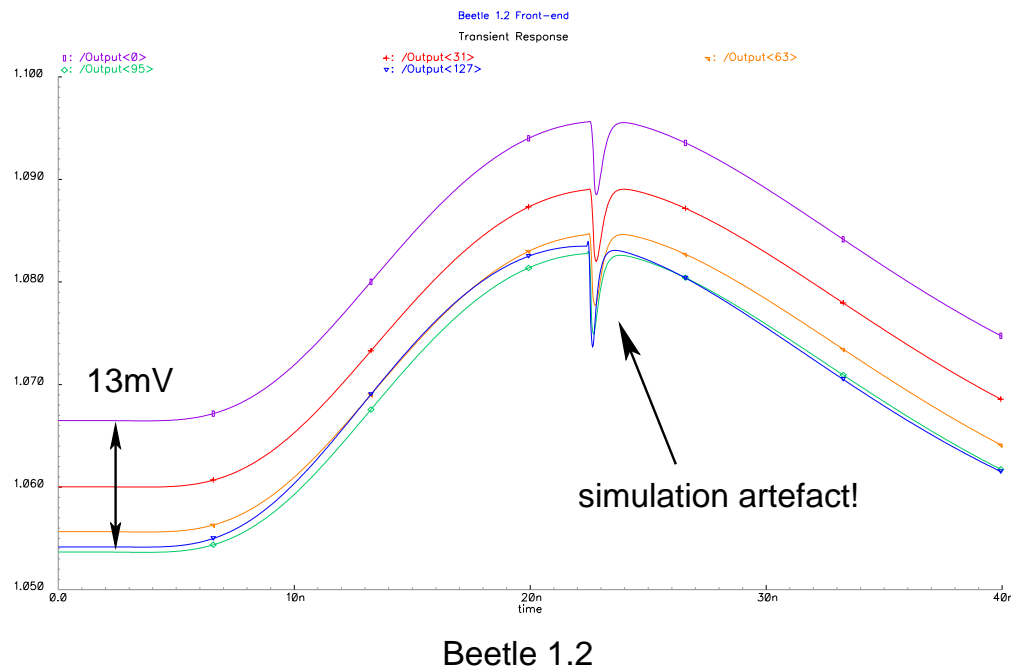- Testpulse, Front-end and Pipeline
- 128 channels
- with channel to channel resitors




Multiplexer

- reduced number of flip-flops (1/3)
- removed bug during a non-readout in binary mode
- fixed header-crosstalk in 32 on 4 ports mode
- fixed switching spikes in header
- two adjustable header sizes (-2 / +2) and (0 / 5)
- new guardring concept to prevent digital crosstalk
- improved power routing (less ohmic)
- analog power separation MUX / Output driver
- digital power separation MUX / digital core
- decoupling capacitors for digital power net

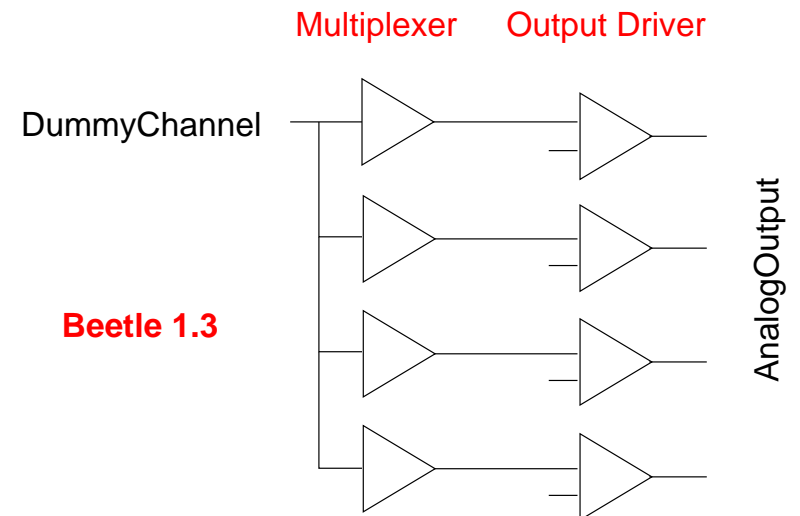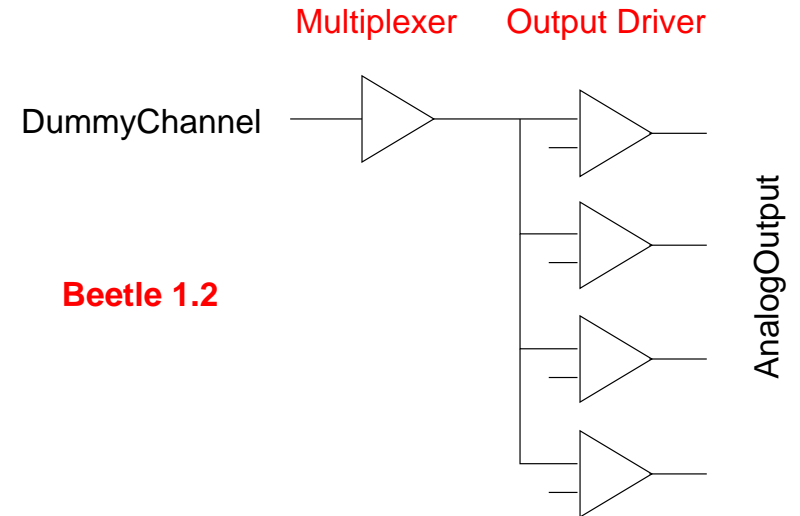


Output Driver

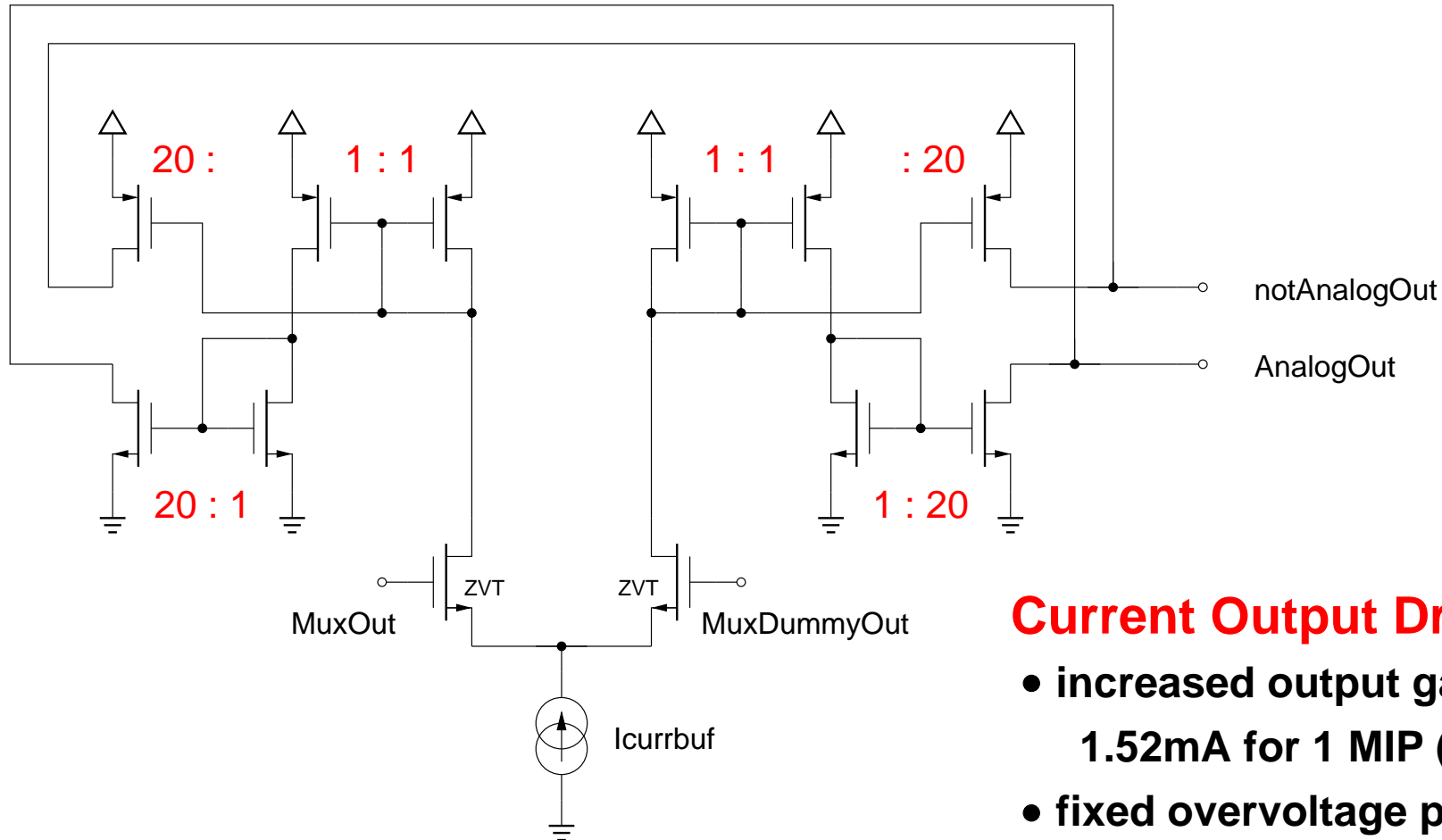

Current Output Driver

- increased output gain by factor 3.2
1.52mA for 1 MIP (22.000e)
- fixed overvoltage problem
- own power supply (pad VddTx)
- improved guardrings


Power Supply / Pads

 

- chip length increased from 5100 μ m to 5400 μ m
- new arrangement of analog power pads
- additional power pads for digital core
- separation of power comparator core / LVDS output driver
- RoTokenIn and RoReTokenIn with int. pulldown
- merged adjacent digital power pads
- I2C pads SCL / SDA now 5V tolerant
- power separation of digital core and multiplexer
- power separation of analog part (MUX/pipeamp) and current output driver
- improved ESD protection
- on chip decoupling capacitors




On-Chip Blocking Capacitors

 




Fix of Sticky Charge Effect


Design Goal

 


N.B.: Pipeamp Settling Time increases

 

Analogue Delay

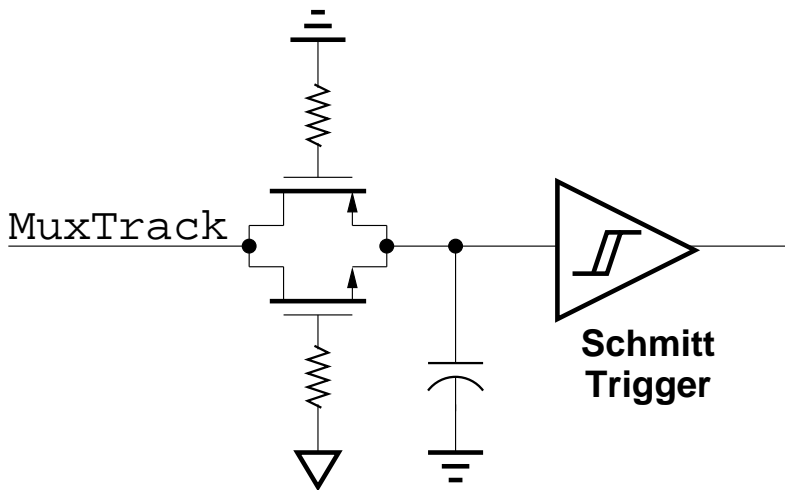


Simulation Results

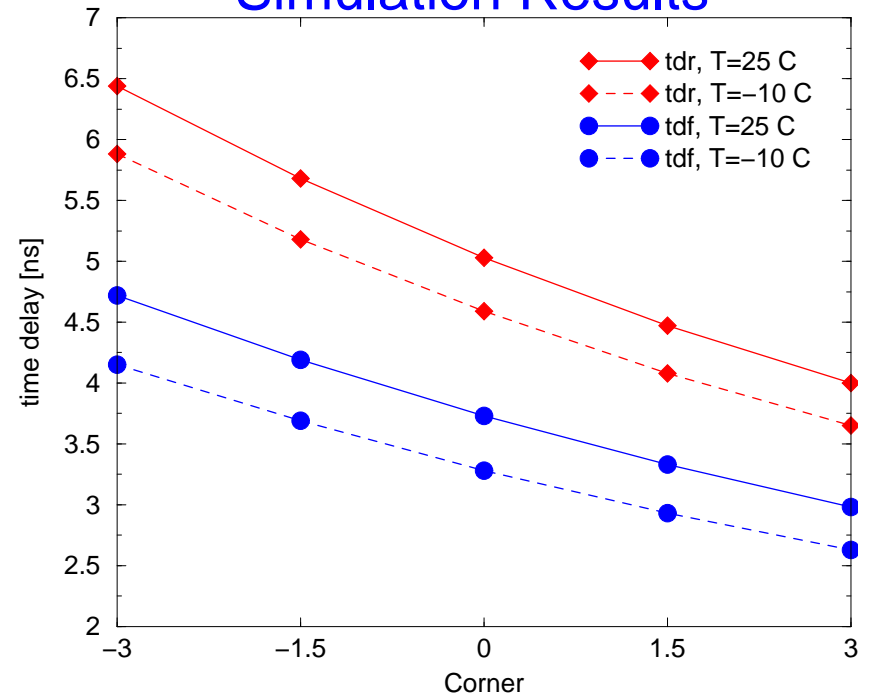



Control Logic: Functional Changes

- ♦ bug fix: daisy chain token handling
last chip in daisy chain (DaisyLast) is no longer sensitive to return token signal (RoReTokenIn)
- ♦ bug fix: operation with $Rclk < 0.5 Sclk$
 - Beetle1.2:** multiple generation of 'ReleaseColumn' signal (depending on $Rclk/Sclk$ ratio) results in FIFO overflow
 - Beetle1.3:** generation of 'ReleaseColumn' signal is independent of $Rclk$ frequency
- ♦ equalising control sequence cons. / non-consec. readout

 




Control Logic: Clock Routing


Topology: clock trunk

layout view of FastControl

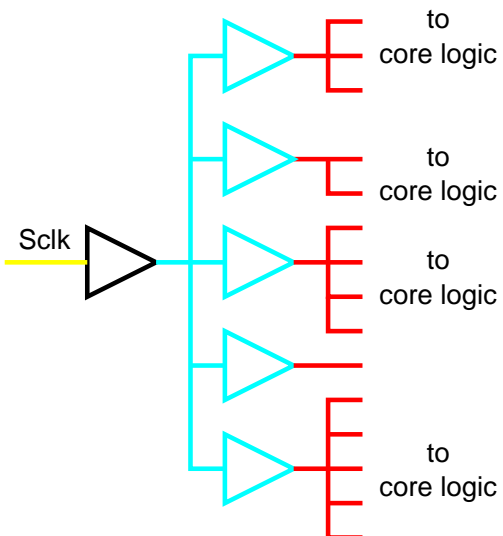

= 104


(on Beetle1.2: # = 275)

 



Control Logic: Power Routing

- merged pad openings of existing power pads: enables 1–2 additional bond wires per pad
- additional power pads at bottom side
- blocking capacitors: 414 (core) + 96 (pads): 1/3 nF
- reduced area of FastControl (– 80 um in y-direction): allows improved power routing

 

Beetle 1.3

Beetle 1.3

- submitted June 2003
- expect to be back: September 2003

