

# Beetle 1.0 - A new Readout Chip for LHCb

Daniel Baumeister, Werner Hofmann, Karl-Tasso Knöpfle,

Sven Löchner, Michael Schmelling, Edgar Sexauer

Max-Planck-Institute for Nuclear Physics Heidelberg

Martin Feuerstack-Raible, Josef Schweda

University of Heidelberg

Niels van Bakel, Jo van den Brand, Hans Verkoijen

NIKHEF Amsterdam

Neville Harnew, Nigel Smale


University of Oxford

## Overview

- Specifications from LHCb
- Architecture of the Beetle 1.0
- Analog stages (simulation and measurements)
- Methods to enhance radiation tolerance
- Layout of the readout chip
- conclusions future plans
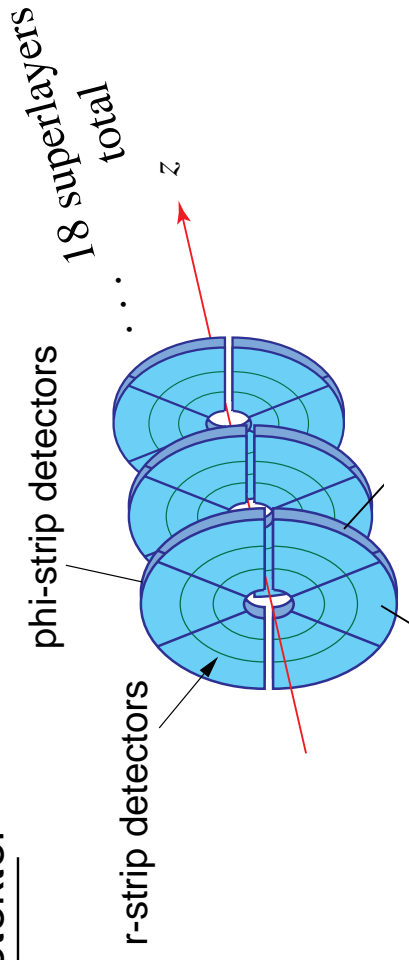
## Goal: Readout Chip for the LHCb Vertex Detektor

- Silicon microstrip detectors (150um)
- 1MIP=11.000 electrons
- 10pF strip capacitance
- single strip occupancy ~3%
- 220.000 channels
- readout pitch: 40 - 60 um



- pipelined analog readout for tracking part of detector
- derive immediate trigger signal for pileup-veto

- Radiation Dose: up to 2MRad/year => 10MRad total dose


Use of the same readout chip in other subdetectors:

- Inner tracker (microstrip gaseous chambers or/and silicon strip detectors)
- RICH backup technology solution (multi anode photo multiplier tubes)


### Key Parameters of Readout Chip:

- Sampling frequency: 40 MHz
- L0 trigger rate: 1MHz
- Readout time per event: 900ns
- Latency (160x25ns) = 4us
- Number of multievent buffer: 16
- deadtimeless readout
  
- max. power consumption: < 4mW/channel
- S/N required by vertex detector: >14
- total accumulated dose: 10 MRad


# Block Diagram of the Beetle 1.0

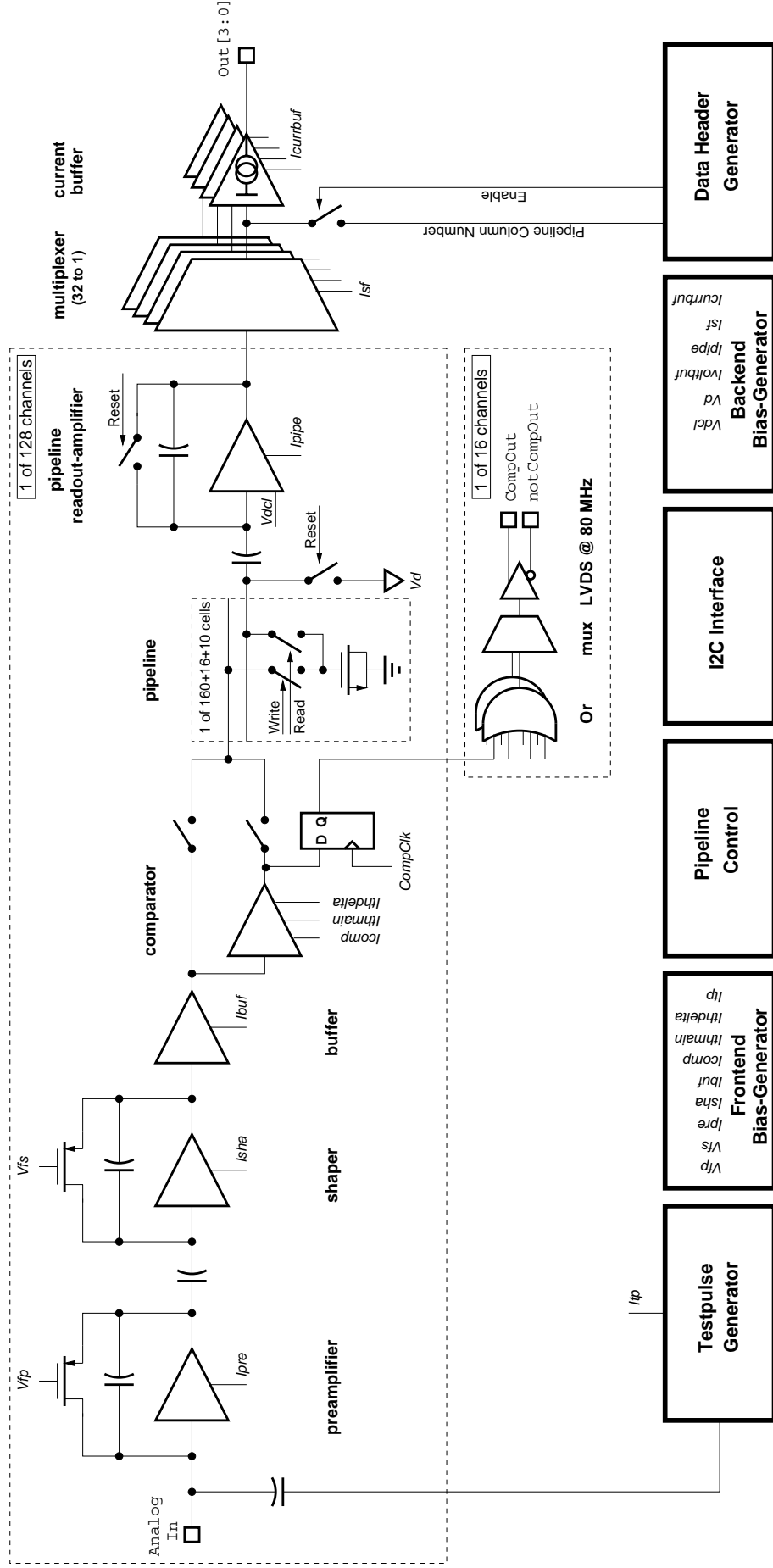

# Frontend Amplifier:

 
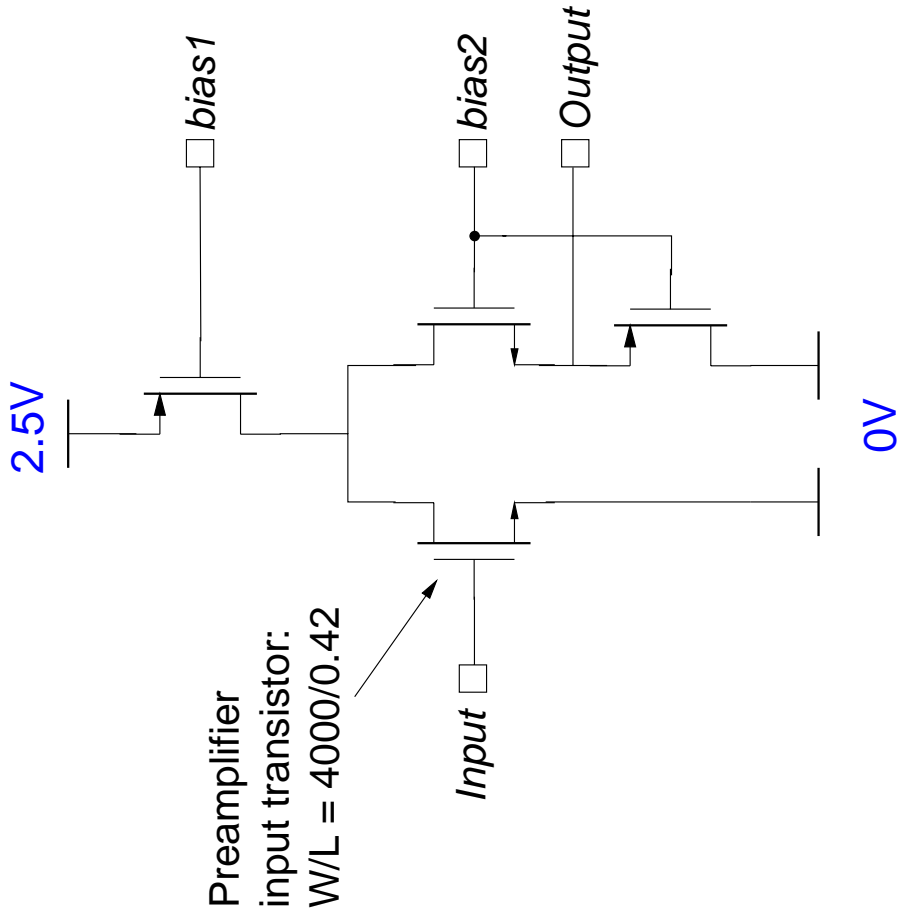
## Core Cell of Preamplifier / Shaper: Folded Cascode Configuration




Measured noise of Frontend  
with testchip:

$$\text{ENC} = 303e + 33.6 \text{ e/pF}$$

at  $I_{\text{preamp}} = 600\mu\text{A}$

total power consumption  
of frontend: 1.88mW / channel

## Measurement with testchip

 


risetime = 25ns

gain = 14.5 mV / 11.000e

remainder after 25ns = 30%

## Simulation of input stage

Transient Response IMIP @ Cload=10pF

 


risetime = 23ns

gain = 14.5 mV / 11.000e

remainder after 25ns = 25%



hp running

 


Dynamic range:  
+- 10 MIP  
(= +- 110.000e)

at power consumption  
of 1.88 mW / channel

peak time does not  
shift for higher signals



## Comparator:

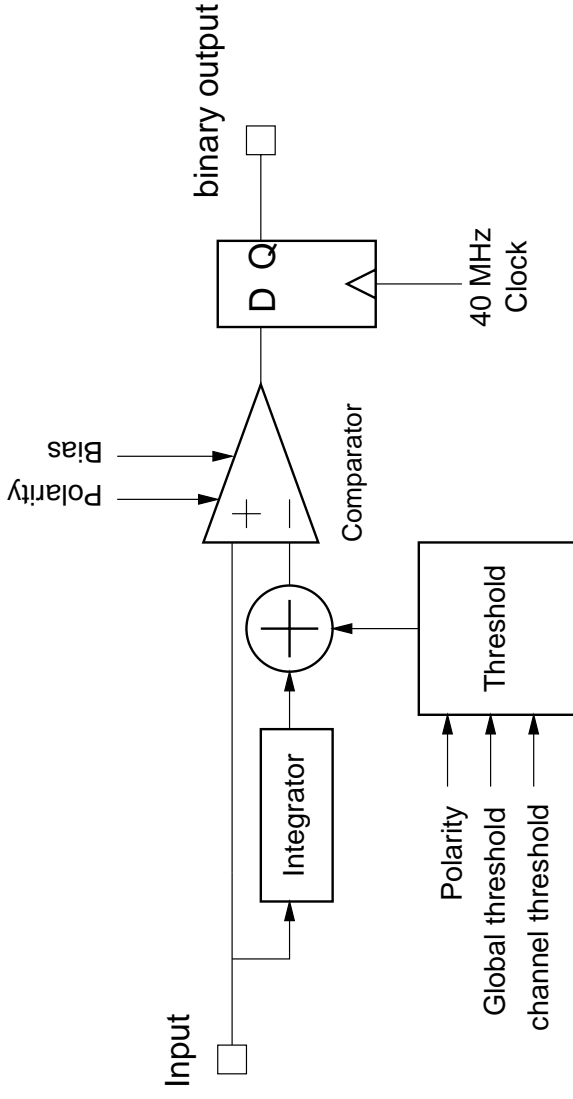

- adjustable threshold for each channel
- binary output:
  - > either stored in pipeline
  - > or imediately brought off chip
- time constant of integrator: 5 $\mu$ s

Analoge Pipeline:

 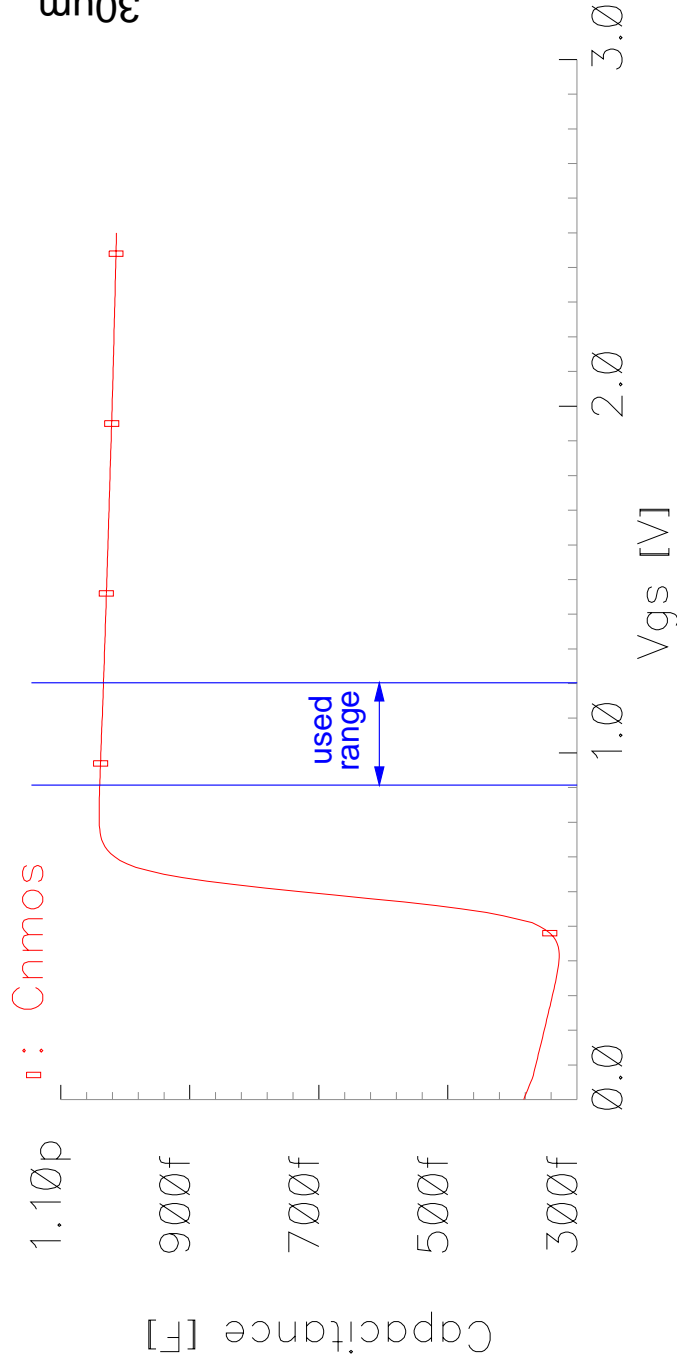- 129 x 186 n-mos gate capacitors
- 2 enclosed n-mos as read/write switch
- Capacitance 1pF




## Pipeline Readout Amplifier:

BeetlePipeamp testPipeamp schematic : Mar 21 23:36:02 2000



Transient Response

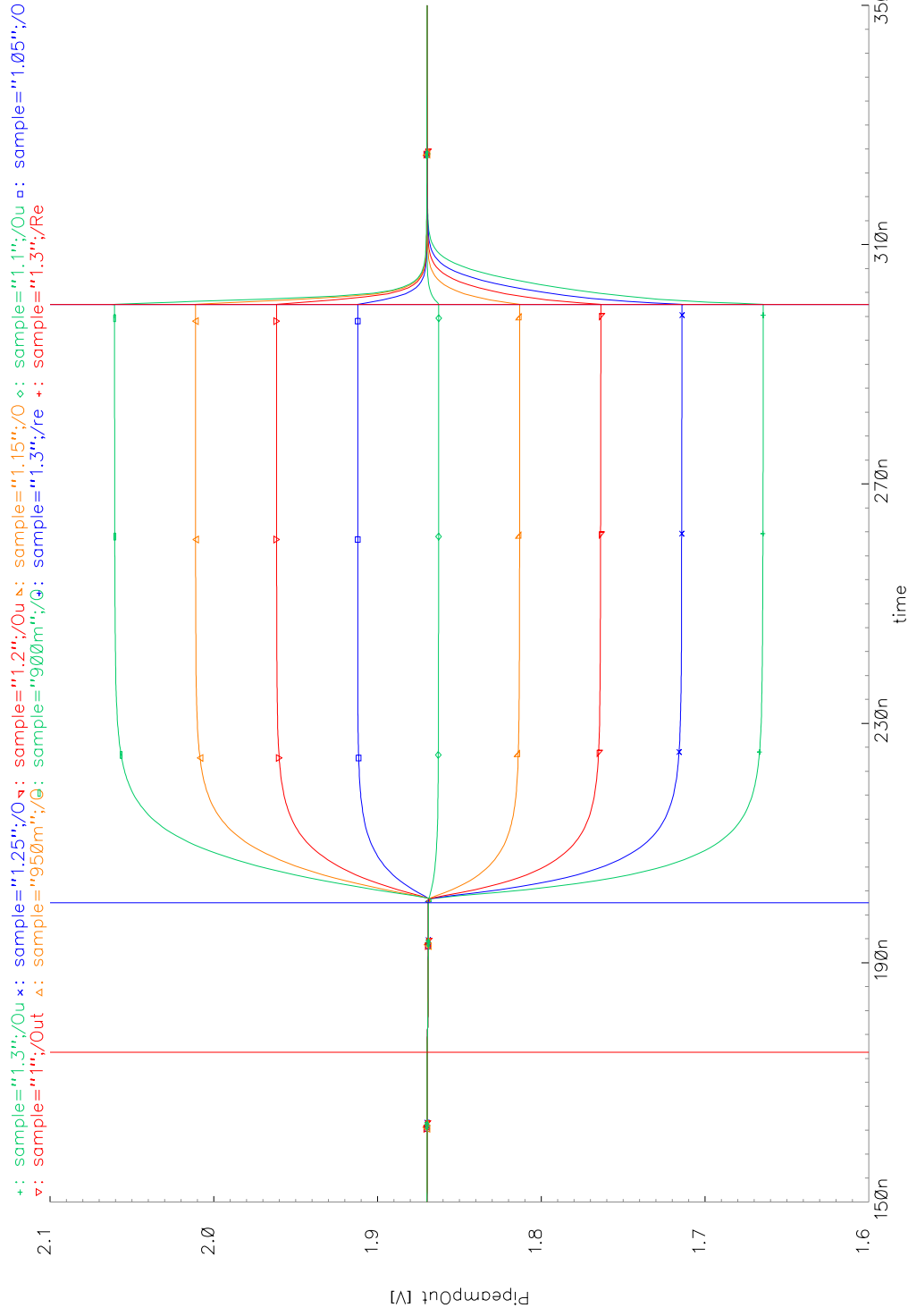

- Resettable charge sensitive amplifier
- Rise time well below 75ns
- folded cascode configuration used as opamp cell

### Multiplexer:

- Sample/Hold stage with source follower
- different multiplexing modes by switching of "Readbit"


1.) 32 channels to 1 output port  
x4

for analog readout at 40MHz  
=>900ns readout time per event

2.) 64 channels to 1 output port:  
x2

for binary readout at 80MHz  
=>900ns readout time per event

 3.) 128 channels to 1 output port  
for analog readout at 40MHz  
=> slow readout for test setups etc.



### Bias Blocks:

- 10bit voltage DACs  
using R2R resistor ladder
- 10 bit current DACs
- reference current using:  
cascoded transistors with  
20k reference resistor  
-> current sources on 20 tested prototype chips  
show spread of < 5%

### Pipeline and Readout Control logic:

- identical to control logic in HELIX128 readout chip
- functional description in Verilog
- Synthesis with Synopsys
- Place and Route using 3 metal layers with Silicon Ensemble
- Size: 1.9mm x 0.8mm

## Slow Control of Readout Chip:

### I2C-Interface:

Assignment of chip address in a self-programming procedure on powerup

### 38 Register write/read

- bias settings for amplifier
- latency
- readout mode
- readout clock frequency programmable

future: parity register

mask register for testpulse, comparator

fail safe token for address generation

different Resets possible (controlled by length of external reset):

- softreset:       resets contents of multievent buffer
- hardreset:       resets trigger & write pointer
- powerupreset:   resets all register contents



## Design techniques to enhance radiation resistance:

- minimize threshold voltage shift by choice of technology
- edgeless n-mos transistor layout to reduce leakage current
- systematic use of guardrings to minimize SEE rate


( *Total Dose and Single Event Effects (SEE) in a 0.25um CMOS Technology*,  
F.Faccio et al. in *CERN/LHCC/98-36* )

- forced bias currents / node voltages not fixed
- passive components used as negative feedback

( e.g. *RD20 or HELIX128*, W. Fallot-Burghardt et al. in *HD-ASIC-33-0697* )

Layout of the Beetle 1.0

5.5mm

 

6.1mm

input  
pitch:  
41um  
->50um  
overall

Summary:

- Based on good experience with 2 testchips, we expect to have a readout chip, which fulfills the LHCb requirements
- If basic functionality is given:
  - > characterization in lab
  - > test with detector as soon as possible
  - > irradiation as soon as possible

Submission of Beetle 1.1 planned for end 2000 / start 2001

## additional features:

- JTAG protocol to enable boundary scan
- parity check of all registers to enable SEU detection
- introduction of mask register for testpulse and comparator
- modification of output current buffer

Find further status reports on:

<http://wwwasic.kip.uni-heidelberg.de/lhcb>